

## Experiment 3

### Combinational Circuits: Structural Modeling using Vivado

#### 1.(a) Truth Table:

a	b	c	x	y
0	0	0	1	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	0
1	0	0	0	0
1	0	1	1	0
1	1	0	0	1
1	1	1	1	1

#### 1.(b) Maximum combinational delay:

Maximum combinational delay from c to x is 9.018.

Maximum combinational delay from b to y is 8.224

#### 1.(c) Resource Utilization:

LUTs: 1

I/Os: 5

2. code:

```
module task2(input a,b,c,  
              output x,y
```

```
);
```

```
assign y = ((~(a&b))^(a | b))&(a | b);
```

```
assign x = (a | b)^(~c);
```

```
endmodule
```